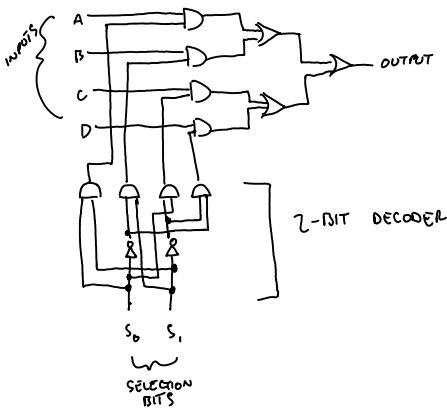


Lab 1 - Practice for Logic Design

Friday, January 29, 2021 10:02 AM

1. Draw a complete schematic diagram of the 4x1 multiplexor, using only three basic gates (2-input AND, 2-input OR, and negator).



2. Assume that signal X is 3 bits wide (x_2, x_1, x_0).
Write logic equations for F1~F4 based on the following functionalities.

- F1: X contains only one 0.
- F2: X contains an even number of 0's.
- F3: X, when interpreted as an unsigned binary number, is less than 4.
- F4: X, when interpreted as a signed (two's complement) number, is negative.

Now, rewrite your logic equation for F2 using only XOR functions.

F1:	x_0	x_1	x_2	Y	
	0	1	1	1	$(\bar{x}_0 \cdot x_1 \cdot x_2) + (x_0 \cdot \bar{x}_1 \cdot x_2) + (x_0 \cdot x_1 \cdot \bar{x}_2)$
	1	0	1	1	
	0	1	1	1	

F2:	x_0	x_1	x_2	Y	
	0	0	1	1	$(x_0 \cdot x_1 \cdot x_2) + (\bar{x}_0 \cdot \bar{x}_1 \cdot x_2) + (\bar{x}_0 \cdot x_1 \cdot \bar{x}_2) + (x_0 \cdot \bar{x}_1 \cdot \bar{x}_2)$
	0	1	0	1	
	1	0	0	1	
	1	1	1	1	

F3:	x_0	x_1	x_2	Y	
	0	0	0	1	$(\bar{x}_0 \cdot \bar{x}_1 \cdot \bar{x}_2) + (\bar{x}_0 \cdot \bar{x}_1 \cdot x_2) + (\bar{x}_0 \cdot x_1 \cdot \bar{x}_2) + (x_0 \cdot x_1 \cdot x_2)$
	0	0	1	1	
	0	1	0	1	$\bar{x}_0 \cdot ((\bar{x}_1 \cdot \bar{x}_2) + (\bar{x}_1 \cdot x_2) + (x_1 \cdot \bar{x}_2) + (x_1 \cdot x_2))$
	0	1	1	1	$\bar{x}_0 \cdot (\bar{x}_1 \cdot (\bar{x}_2 + x_2) + x_1 \cdot (\bar{x}_2 + x_2))$
					$\bar{x}_0 \cdot (\bar{x}_1 + x_1)$
					\bar{x}_0

F4:	x_0	x_1	x_2	Y	
	1	0	0	1	$(x_0 \cdot \bar{x}_1 \cdot \bar{x}_2) + (x_0 \cdot \bar{x}_1 \cdot x_2) + (x_0 \cdot x_1 \cdot \bar{x}_2) + (x_0 \cdot x_1 \cdot x_2)$
	1	0	1	1	
	1	1	0	1	$x_0 \cdot ((\bar{x}_1 \cdot \bar{x}_2) + (\bar{x}_1 \cdot x_2) + (x_1 \cdot \bar{x}_2) + (x_1 \cdot x_2))$
	1	1	1	1	$x_0 \cdot (\bar{x}_1 \cdot (\bar{x}_2 + x_2) + x_1 \cdot (\bar{x}_2 + x_2))$
					$x_0 \cdot (\bar{x}_1 + x_1)$
					x_0

F2:	x_0	x_1	x_2	Y	
w/ XOR	0	0	1	1	$x_0 \oplus x_1 \oplus x_2$
	0	1	0	1	
	1	0	0	1	
	1	1	1	1	

3. Consider the following two equivalent logic equations for E.


$$E = ((A \cdot B) + (A \cdot C) + (B \cdot C)) \cdot (\overline{A \cdot B \cdot C})$$

$$E = (A \cdot B \cdot \overline{C}) + (A \cdot \overline{B} \cdot C) + (\overline{A} \cdot B \cdot C)$$


Draw a schematic diagram for each equation with minimum number of 2-input gates.

Answer which equation is more efficient in terms of the number of 2-input gates.

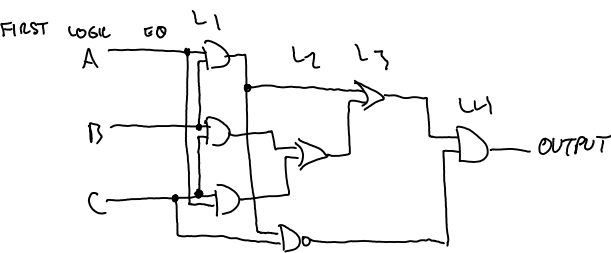Note that the negator is not counted for this.



SECOND LOGIC EQ

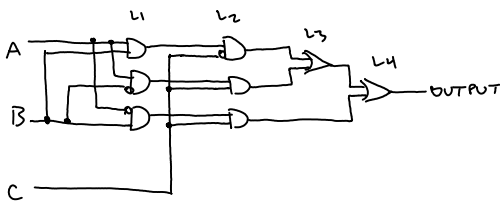

THE FIRST LOGIC EQUATION IS MORE EFFICIENT.
WHILE BOTH EQUATIONS USE 4-LEVEL LOGIC TIME
FIRST LOGIC EQUATION CAN BE BUILT W 7
GATES WHILE THE SECOND REQUIRES 8.

4. Prove that the two equations for E (shown in #3) are equivalent by using DeMorgan's laws and other basic laws (if needed).

$$\begin{aligned} (A \cdot B \cdot \bar{C}) + (A \cdot \bar{B} \cdot C) + (\bar{A} \cdot B \cdot C) &= ((A \cdot B) + (A \cdot C) + (B \cdot C)) \cdot \overline{(A \cdot B \cdot C)} \\ &= ((A \cdot B) + (A \cdot C) + (B \cdot C)) \cdot (\bar{A} + \bar{B} + \bar{C}) \\ &= (((A \cdot B) \cdot (\bar{A} + \bar{B} + \bar{C})) + ((A \cdot C) \cdot (\bar{A} + \bar{B} + \bar{C})) + ((B \cdot C) \cdot (\bar{A} + \bar{B} + \bar{C}))) \\ &= (((A \cdot \bar{A} \cdot B) + (A \cdot \bar{B} \cdot B) + (A \cdot B \cdot \bar{C})) + ((A \cdot \bar{C} \cdot A) + (A \cdot C \cdot \bar{B}) + (A \cdot C \cdot \bar{C})) + ((B \cdot C \cdot \bar{A}) + (B \cdot C \cdot \bar{B}) + (B \cdot C \cdot \bar{C}))) \\ &= ((0 + 0 + \cancel{A \cdot B}) + (0 + \cancel{A \cdot C} + 0) + (\cancel{B \cdot C} + 0 + 0)) \\ &= (A \cdot B \cdot \bar{C}) + (A \cdot \bar{B} \cdot C) + (\bar{A} \cdot B \cdot C) \end{aligned}$$

∴ EQUIVALENT

5. One logic function that is used for a variety of purposes is *exclusive_OR (XOR)*. The output of the 2-input XOR function is true only if exactly one of the inputs is true. Prove that the following two logic equations for the 2-input XOR function is equivalent by using the DeMorgan's laws and other basic laws (if needed).

$$\begin{aligned} \text{XOR} &= (A \cdot \bar{B}) + (\bar{A} \cdot B) \\ \text{XOR} &= (A+B) \cdot \overline{(A \cdot B)} \end{aligned}$$

$$\begin{aligned} (A \cdot \bar{B}) + (\bar{A} \cdot B) &= (A+B) \cdot \overline{(A \cdot B)} \\ &= (A+B) \cdot (\bar{A} + \bar{B}) \\ &= (\bar{A} \cdot (A+B)) + (\bar{B} \cdot (A+B)) \\ &= (\underbrace{A \cdot \bar{A}}_0 + \bar{A} \cdot B) + (A \cdot \bar{B} + \underbrace{B \cdot \bar{B}}_0) \\ &= (\bar{A} \cdot B) + (A \cdot \bar{B}) \end{aligned}$$

∴ EQUIVALENT

6. From #5, extend your practice to the 3-input XOR function by showing its truth table, logic equation and schematic diagram (using only 2-input basic gates).

A	B	C	A⊕B	(A⊕B)⊕C
0	0	0	0	0
0	0	1	0	1
0	1	0	1	1
0	1	1	1	0
1	0	0	1	1
1	0	1	1	0
1	1	0	0	0
1	1	1	0	1

$$(\bar{A} \cdot \bar{B} \cdot C) + (\bar{A} \cdot B \cdot \bar{C}) + (A \cdot \bar{B} \cdot \bar{C}) + (A \cdot B \cdot C)$$

